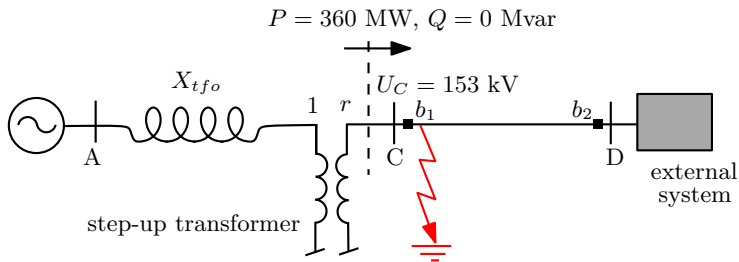


The system shown below has the following characteristics:

- transmission line C-D: 30 km, nominal voltage 150 kV, $r = 0.05 \Omega/\text{km}$,
 $x = 0.32 \Omega/\text{km}$, shunt susceptance neglected
- generator (bus A): nominal power 400 MVA, nominal voltage 15 kV, $X'' = 0.17 \text{ pu}^1$
- step-up transformer A-C: nominal power 400 MVA, leakage reactance $X_{tfo} = 0.16 \text{ pu}$,
ratio $r = 1.03 \text{ pu}/\text{pu}^2$
- external system (bus D) : short-circuit power 9 000 MVA.

The operating point is shown in the figure.



¹on the (15 kV, 400 MVA) base

²on the (15 kV, 150kV, 400 MVA) bases

A three-phase short-circuit without resistance takes place on the line, at a negligible distance from the switching station of bus C.

Determine :

- 1 the currents in the circuit breakers b_1 and b_2
- 2 the short-circuit power at bus C
- 3 the same when the generator is not in operation
- 4 the voltage at buses A and D during the short-circuit.